

$91\text{m}\Omega$

$96\text{k}\Omega$

$U_7$

+

-

$50\Omega$

$26\Omega$

$I_6$

-

$54\text{k}\Omega$

$U_4$

+

$53\text{mV}$

+

+

$32\text{V}$

-

